

Computer Architecture

Project: MIPS 32 Processor Implementation
Single-Cycle and Pipelined Architectures

Problem: Sum of powers of 2 within an interval $[a, b]$

Student:

Măgerușan Alexandru

Date:

May 23, 2026

Contents

1	Introduction	2
2	Solution Algorithm	2
2.1	C++ Source Code	2
2.2	x86 Assembly Code	3
2.3	MIPS Assembly Code	4
3	Machine Code and ROM Mapping	5
I	Single-Cycle Implementation	6
4	Instruction Set and Control Signals	6
4.1	Instruction Classification and Datapath	6
4.1.1	R-Type Instructions (Register)	6
4.1.2	I-Type Instructions (Immediate)	6
4.1.3	J-Type Instructions (Jump)	8
5	Hardware Components and Architecture	8
5.1	Processor Block Diagram	8
5.2	IFetch.vhd	9
5.3	IDecode.vhd	10
5.4	EX.vhd	11
5.5	MEM.vhd	12
5.6	UC.vhd	13
5.7	test_env.vhd	14
6	Single-Cycle Execution Trace	17
II	Pipelined Implementation	18
7	Pipeline Registers and Architecture	18
8	Pipeline Control Signals	19
9	Hazard Resolution	19
10	Pipeline Execution Trace	20
10.1	Ideal Execution (Hazard Identification)	20
11	VHDL Code Modifications (Pipeline)	23
III	Conclusions	26
12	FPGA Synthesis	26

1 Introduction

This project presents the hardware design of a 32-bit MIPS microprocessor implemented in VHDL. The implementation is divided into two distinct evolutionary phases:

- **Phase 1:** A foundational Single-Cycle architecture.
- **Phase 2:** An advanced 5-stage Pipelined architecture with hazard resolution.

The system is validated by solving a specific problem: calculating the sum of powers of 2 from a given dataset, conditionally restricted to a specified interval.

2 Solution Algorithm

2.1 C++ Source Code

High-level reference implementation of the algorithm.

```
1  #include <stdio.h>
2
3  int main()
4  {
5      int a = 2;
6      int b = 90;
7      int x[] = {0, 1, 2, 3, 256, 14, 16};
8      int n = 7;
9
10     int sum = 0;
11     int i = -1;
12
13     while (i < n - 1)
14     {
15         i++;
16         int val = x[i];
17
18         if (val < a) continue;
19         if (val > b) continue;
20         if (val <= 0) continue;
21
22         int temp = val - 1;
23         int test = val & temp;
24
25         if (test != 0) continue;
26
27         sum = sum + val;
28     }
29
30     printf("Sum:%d\n", sum);
31     return 0;
32 }
```

C++ Reference Program

2.2 x86 Assembly Code

Generated x86 code for testing the processing logic.

```
1 main:
2     push    rbp
3     mov     rbp, rsp
4     mov     DWORD PTR [rbp-12], 2
5     mov     DWORD PTR [rbp-16], 90
6     mov     DWORD PTR [rbp-64], 0
7     mov     DWORD PTR [rbp-60], 1
8     mov     DWORD PTR [rbp-56], 2
9     mov     DWORD PTR [rbp-52], 3
10    mov     DWORD PTR [rbp-48], 256
11    mov     DWORD PTR [rbp-44], 14
12    mov     DWORD PTR [rbp-40], 16
13    mov     DWORD PTR [rbp-20], 7
14    mov     DWORD PTR [rbp-4], 0
15    mov     DWORD PTR [rbp-8], -1
16    jmp     .L2
17 .L7:
18    add     DWORD PTR [rbp-8], 1
19    mov     eax, DWORD PTR [rbp-8]
20    cdqe
21    mov     eax, DWORD PTR [rbp-64+rax*4]
22    mov     DWORD PTR [rbp-24], eax
23    mov     eax, DWORD PTR [rbp-24]
24    cmp     eax, DWORD PTR [rbp-12]
25    jge     .L3
26    jmp     .L2
27 .L3:
28    mov     eax, DWORD PTR [rbp-24]
29    cmp     eax, DWORD PTR [rbp-16]
30    jle     .L4
31    jmp     .L2
32 .L4:
33    cmp     DWORD PTR [rbp-24], 0
34    jg      .L5
35    jmp     .L2
36 .L5:
37    mov     eax, DWORD PTR [rbp-24]
38    sub     eax, 1
39    mov     DWORD PTR [rbp-28], eax
40    mov     eax, DWORD PTR [rbp-24]
41    and     eax, DWORD PTR [rbp-28]
42    mov     DWORD PTR [rbp-32], eax
43    cmp     DWORD PTR [rbp-32], 0
44    je      .L6
45    jmp     .L2
46 .L6:
47    mov     eax, DWORD PTR [rbp-24]
48    add     DWORD PTR [rbp-4], eax
49 .L2:
50    mov     eax, DWORD PTR [rbp-20]
51    sub     eax, 1
52    cmp     DWORD PTR [rbp-8], eax
53    jl      .L7
54    mov     eax, 0
55    pop     rbp
56    ret
```

x86 Assembly Code

2.3 MIPS Assembly Code

Final implementation intended for execution on the MIPS processor.

```
1  .data
2      # Declare the array in memory (each number occupies 1 word = 4 bytes)
3      x: .word 0, 1, 2, 3, 256, 14, 16
4
5  .text
6  .globl main
7  main:
8      addi $1, $0, 2      # a = 2
9      addi $2, $0, 90     # b = 90
10     addi $3, $0, 7      # n = 7
11     la    $4, x          # base_addr = starting address of array x
12     add   $5, $0, $0     # sum = 0
13     add   $6, $0, $0     # i = 0
14
15 loop_start:
16     slt   $7, $6, $3     # $7 = 1 if i < n
17     beq   $7, $0, end     # If i >= n, done, jump to 'end'
18
19     # --- ADDRESS CORRECTION ---
20     sll   $9, $6, 2      # $9 = i * 4
21     add   $9, $4, $9     # $9 = address of current element
22     lw    $8, 0($9)     # val = read x[i] into $8
23
24     addi  $6, $6, 1      # i = i + 1
25
26     # Check: val < a
27     slt   $7, $8, $1     # $7 = 1 if val < a
28     bne   $7, $0, loop_start
29
30     # Check: val > b
31     slt   $7, $2, $8     # $7 = 1 if b < val
32     bne   $7, $0, loop_start
33
34     # Check: val > 0
35     slt   $7, $0, $8     # $7 = 1 if 0 < val
36     beq   $7, $0, loop_start
37
38     # Check: is it a power of 2? (val & (val - 1) == 0)
39     addi  $9, $8, -1     # $9 = val - 1
40     and   $9, $8, $9     # $9 = val & (val - 1)
41     bne   $9, $0, loop_start
42
43     # Add to sum
44     add   $5, $5, $8     # sum = sum + val
45     j     loop_start
46
47 end:
48     addi  $v0, $0, 10    # exit
49     syscall
```

MIPS Assembly Code for the processor

3 Machine Code and ROM Mapping

The following table details the binary and hexadecimal translation of the MIPS Assembly code, as inserted into the instruction memory (ROM) for both architectures.

PC	Machine Code (Binary)	Hex	MIPS ASM
0	001000_00000_00001_00000000000000010	20010002	addi \$1, \$0, 2
1	001000_00000_00010_00000000001011010	2002005A	addi \$2, \$0, 90
2	001000_00000_00011_00000000000000111	20030007	addi \$3, \$0, 7
3	000000_00000_00000_00100_00000_100000	00002020	add \$4, \$0, \$0 (<i>la \$4, x</i>)
4	000000_00000_00000_00101_00000_100000	00002820	add \$5, \$0, \$0
5	000000_00000_00000_00110_00000_100000	00003020	add \$6, \$0, \$0
— <i>loop_start</i> : (<i>PC</i> = 6) —			
6	000000_00110_00011_00111_00000_101010	00C3382A	slt \$7, \$6, \$3
7	000100_00111_00000_00000000000001111	10E0000F	beq \$7, \$0, end (<i>+15</i>)
8	000000_00000_00110_01001_00010_000000	00064880	sll \$9, \$6, 2
9	000000_00100_01001_01001_00000_100000	00894820	add \$9, \$4, \$9
10	100011_01001_01000_00000000000000000	8D280000	lw \$8, 0(\$9)
11	001000_00110_00110_00000000000000001	20C60001	addi \$6, \$6, 1
12	000000_01000_00001_00111_00000_101010	0101382A	slt \$7, \$8, \$1
13	000101_00111_00000_11111111111111000	14E0FFF8	bne \$7, \$0, loop_start (<i>-8</i>)
14	000000_00010_01000_00111_00000_101010	0048382A	slt \$7, \$2, \$8
15	000101_00111_00000_11111111111110110	14E0FFF6	bne \$7, \$0, loop_start (<i>-10</i>)
16	000000_00000_01000_00111_00000_101010	0008382A	slt \$7, \$0, \$8
17	000100_00111_00000_11111111111110100	10E0FFF4	beq \$7, \$0, loop_start (<i>-12</i>)
18	001000_01000_01001_11111111111111111	2109FFFF	addi \$9, \$8, -1
19	000000_01000_01001_01001_00000_100100	01094824	and \$9, \$8, \$9
20	000101_01001_00000_11111111111110001	1520FFF1	bne \$9, \$0, loop_start (<i>-15</i>)
21	000000_00101_01000_00101_00000_100000	00A82820	add \$5, \$5, \$8
22	000010_0000000000000000000000000110	08000006	j loop_start (<i>Imp target 6</i>)
— <i>end</i> : (<i>PC</i> = 23) —			
23	001000_00000_00010_00000000000001010	2002000A	addi \$v0, \$0, 10 (<i>\$v0 is \$2</i>)
24	000000_00000_00000_00000_00000_001100	0000000C	syscall (<i>generic syscall code</i>)

Table 1: Detailed mapping between source code and ROM memory

Part I

Single-Cycle Implementation

This part details the initial implementation of the processor, where each instruction executes completely within a single clock cycle.

4 Instruction Set and Control Signals

The processor decodes a subset of 10 MIPS 32 instructions. The following table presents the binary encodings and signals generated by the Control Unit (UC).

Instruction	Opcode [31-26]	RegDst	ExtOp	ALUSrc	Branch	Br_ne	Jump	MemWrite	MemtoReg	RegWrite	ALUOp[1:0]	function [5-0]	ALUCtrl[2:0]
add	000000	1	0	0	0	0	0	0	0	1	10	100000	000 (+)
and	000000	1	0	0	0	0	0	0	0	1	10	100100	010 (&)
slt	000000	1	0	0	0	0	0	0	0	1	10	101010	011 (<)
sll	000000	1	0	0	0	0	0	0	0	1	10	000000	100 (<<)
addi	001000	0	1	1	0	0	0	0	0	1	00 (+)	X	000 (+)
lw	100011	0	1	1	0	0	0	0	1	1	00 (+)	X	000 (+)
sw	101011	0	1	1	0	0	0	1	0	0	00 (+)	X	000 (+)
beq	000100	0	1	0	1	0	0	0	0	0	01 (-)	X	001 (-)
bne	000101	0	1	0	0	1	0	0	0	0	01 (-)	X	001 (-)
j	000010	0	0	0	0	0	1	0	0	0	00	X	000

Table 2: Instruction encodings and control signals

4.1 Instruction Classification and Datapath

4.1.1 R-Type Instructions (Register)

Uses three registers: sources *rs*, *rt* and destination *rd*. The ALU performs the operation indicated by *funct*.

 


Figure 1: Datapath for R-Type instructions

4.1.2 I-Type Instructions (Immediate)

Uses a 16-bit immediate constant, extended to 32 bits (sign or zero) before entering the ALU.

 


Figure 2: Sign Extend (addi)

 


Figure 3: Zero Extend

Memory Access (lw and sw) The memory address is the sum of the base register and the sign-extended offset.

 


Figure 4: Load (lw)

 


Figure 5: Store (sw)

Conditional Branch (beq, bne) The branch decision is based on checking operand equality in the ALU.

 


Figure 6: Branch instructions

4.1.3 J-Type Instructions (Jump)

Directly modifies the Program Counter with the provided address.

 


Figure 7: Jump instructions

5 Hardware Components and Architecture

5.1 Processor Block Diagram

The diagram illustrates the interconnection of the IFetch, IDecode, EX, and MEM modules. It was logically extended to support the `bne` instruction.

 


Figure 8: MIPS Single-Cycle Architecture

5.2 IFetch.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity IFetch is
6      Port ( clk          : in  STD_LOGIC;
7            rst          : in  STD_LOGIC;
8            en           : in  STD_LOGIC;
9            BranchAddress : in  STD_LOGIC_VECTOR (31 downto 0);
10           JumpAddress  : in  STD_LOGIC_VECTOR (31 downto 0);
11           Jump         : in  STD_LOGIC;
12           PCSrc        : in  STD_LOGIC;
13           Instruction   : out STD_LOGIC_VECTOR (31 downto 0);
14           PC_plus_4     : out STD_LOGIC_VECTOR (31 downto 0));
15 end IFetch;
16
17 architecture Behavioral of IFetch is
18     signal PC          : STD_LOGIC_VECTOR(31 downto 0) := (others => '0');
19     signal Next_PC     : STD_LOGIC_VECTOR(31 downto 0);
20     signal PC4         : STD_LOGIC_VECTOR(31 downto 0);
21     type rom_type is array (0 to 31) of std_logic_vector(31 downto 0);
22     signal ROM : rom_type := (
23         0 => B"000000_00000_00000_00100_00000_100000",
24         1 => B"001000_00000_01010_00000000000010000",
25         2 => B"100011_00100_00001_00000000000000000",
26         3 => B"100011_00100_00010_000000000000000100",
27         4 => B"100011_00100_00011_0000000000000001000",
28         5 => B"000000_00000_00000_00101_00000_100000",
29         6 => B"000000_00000_00000_00110_00000_100000",
30         7 => B"000000_00110_00011_00111_00000_101010",
31         8 => B"000100_00111_00000_00000000000001111",

```

```

32     9  => B"000000_00000_00110_01001_00010_000000",
33     10 => B"000000_01010_01001_01001_00000_100000",
34     11 => B"100011_01001_01000_0000000000000000",
35     12 => B"001000_00110_00110_0000000000000001",
36     13 => B"000000_01000_00001_00111_00000_101010",
37     14 => B"000101_00111_00000_1111111111111000",
38     15 => B"000000_00010_01000_00111_00000_101010",
39     16 => B"000101_00111_00000_1111111111110110",
40     17 => B"000000_00000_01000_00111_00000_101010",
41     18 => B"000100_00111_00000_1111111111110100",
42     19 => B"001000_01000_01001_1111111111111111",
43     20 => B"000000_01000_01001_01001_00000_100100",
44     21 => B"000101_01001_00000_1111111111110001",
45     22 => B"000000_00101_01000_00101_00000_100000",
46     23 => B"000010_0000000000000000000000000111",
47     24 => B"101011_00100_00101_00000000000001100",
48     25 => B"000010_000000000000000000000000011001",
49     others => B"000000_00000_00000_00000_00000_000000"
50 );
51 begin
52     process(clk, rst)
53     begin
54         if rst = '1' then
55             PC <= (others => '0');
56         elsif rising_edge(clk) then
57             if en = '1' then
58                 PC <= Next_PC;
59             end if;
60         end if;
61     end process;
62
63     PC4 <= PC + 4;
64     PC_plus_4 <= PC4;
65     Next_PC <= JumpAddress when Jump = '1' else
66         BranchAddress when PCSrc = '1' else
67         PC4;
68     Instruction <= ROM(conv_integer(PC(6 downto 2)));
69 end Behavioral;

```

5.3 IDcode.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity IDcode is
6      Port ( clk          : in  STD_LOGIC;
7            en            : in  STD_LOGIC;
8            Instr         : in  STD_LOGIC_VECTOR (25 downto 0);
9            WD            : in  STD_LOGIC_VECTOR (31 downto 0);
10           RegWrite      : in  STD_LOGIC;
11           RegDst        : in  STD_LOGIC;
12           ExtOp         : in  STD_LOGIC;
13           RD1           : out STD_LOGIC_VECTOR (31 downto 0);
14           RD2           : out STD_LOGIC_VECTOR (31 downto 0);
15           Ext_Imm       : out STD_LOGIC_VECTOR (31 downto 0);
16           func          : out STD_LOGIC_VECTOR (5 downto 0);
17           sa            : out STD_LOGIC_VECTOR (4 downto 0));
18 end IDcode;

```

```

19
20 architecture Behavioral of IDecode is
21     type reg_array is array(0 to 31) of STD_LOGIC_VECTOR(31 downto 0);
22     signal reg_file : reg_array := (others => x"00000000");
23     signal WriteAddress : STD_LOGIC_VECTOR(4 downto 0);
24 begin
25     WriteAddress <= Instr(15 downto 11) when RegDst = '1' else Instr(20
        downto 16);
26     process(clk)
27     begin
28         if rising_edge(clk) then
29             if en = '1' and RegWrite = '1' then
30                 reg_file(conv_integer(WriteAddress)) <= WD;
31             end if;
32         end if;
33     end process;
34
35     RD1 <= reg_file(conv_integer(Instr(25 downto 21)));
36     RD2 <= reg_file(conv_integer(Instr(20 downto 16)));
37     Ext_Imm(15 downto 0) <= Instr(15 downto 0);
38     Ext_Imm(31 downto 16) <= (others => Instr(15)) when ExtOp = '1' else (
        others => '0');
39     func <= Instr(5 downto 0);
40     sa <= Instr(10 downto 6);
41 end Behavioral;

```

5.4 EX.vhd

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_UNSIGNED.ALL;
4 use IEEE.NUMERIC_STD.ALL;
5
6 entity EX is
7     Port ( PC_plus_4      : in  STD_LOGIC_VECTOR (31 downto 0);
8           RD1             : in  STD_LOGIC_VECTOR (31 downto 0);
9           RD2             : in  STD_LOGIC_VECTOR (31 downto 0);
10          Ext_Imm          : in  STD_LOGIC_VECTOR (31 downto 0);
11          ALUSrc           : in  STD_LOGIC;
12          ALUOp            : in  STD_LOGIC_VECTOR (1 downto 0);
13          func             : in  STD_LOGIC_VECTOR (5 downto 0);
14          sa               : in  STD_LOGIC_VECTOR (4 downto 0);
15          BranchAddress    : out STD_LOGIC_VECTOR (31 downto 0);
16          ALURes           : out STD_LOGIC_VECTOR (31 downto 0);
17          Zero             : out STD_LOGIC);
18 end EX;
19
20 architecture Behavioral of EX is
21     signal ALUCtrl : STD_LOGIC_VECTOR(2 downto 0);
22     signal A, B    : STD_LOGIC_VECTOR(31 downto 0);
23     signal ALU_Out : STD_LOGIC_VECTOR(31 downto 0);
24 begin
25     BranchAddress <= PC_plus_4 + (Ext_Imm(29 downto 0) & "00");
26     A <= RD1;
27     B <= Ext_Imm when ALUSrc = '1' else RD2;
28
29     process(ALUOp, func)
30     begin
31         case ALUOp is

```

```

32     when "00" => ALUCtrl <= "000";
33     when "01" => ALUCtrl <= "001";
34     when "10" =>
35         case func is
36             when "100000" => ALUCtrl <= "000";
37             when "100100" => ALUCtrl <= "010";
38             when "101010" => ALUCtrl <= "011";
39             when "000000" => ALUCtrl <= "100";
40             when others => ALUCtrl <= "000";
41         end case;
42     when others => ALUCtrl <= "000";
43 end case;
44 end process;
45
46 process(A, B, ALUCtrl, sa)
47 begin
48     case ALUCtrl is
49         when "000" => ALU_Out <= A + B;
50         when "001" => ALU_Out <= A - B;
51         when "010" => ALU_Out <= A and B;
52         when "011" =>
53             if signed(A) < signed(B) then ALU_Out <= x"00000001";
54             else ALU_Out <= x"00000000"; end if;
55         when "100" => ALU_Out <= to_stdlogicvector(to_bitvector(B) sll
56             conv_integer(sa));
57         when others => ALU_Out <= (others => '0');
58     end case;
59 end process;
60
61 ALURes <= ALU_Out;
62 Zero <= '1' when ALU_Out = x"00000000" else '0';
63 end Behavioral;

```

5.5 MEM.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity MEM is
6      Port ( clk          : in  STD_LOGIC;
7            en            : in  STD_LOGIC;
8            MemWrite      : in  STD_LOGIC;
9            ALUResin      : in  STD_LOGIC_VECTOR (31 downto 0);
10           RD2           : in  STD_LOGIC_VECTOR (31 downto 0);
11           MemData       : out STD_LOGIC_VECTOR (31 downto 0);
12           ALUResout     : out STD_LOGIC_VECTOR (31 downto 0));
13 end MEM;
14
15 architecture Behavioral of MEM is
16     type ram_type is array (0 to 63) of STD_LOGIC_VECTOR(31 downto 0);
17     signal RAM : ram_type := (
18         0 => x"00000002", -- RAM[0]: a = 2
19         1 => x"0000005A", -- RAM[4]: b = 90
20         2 => x"00000007", -- RAM[8]: n = 7
21         3 => x"00000000", -- RAM[12]: sum = 0
22         4 => x"00000000", -- RAM[16]: x[0] = 0
23         5 => x"00000001", -- RAM[20]: x[1] = 1
24         6 => x"00000002", -- RAM[24]: x[2] = 2

```

```

25     7 => x"00000003", -- RAM[28]: x[3] = 3
26     8 => x"00000100", -- RAM[32]: x[4] = 256
27     9 => x"0000000E", -- RAM[36]: x[5] = 14
28     10 => x"00000010", -- RAM[40]: x[6] = 16
29     others => x"00000000"
30 );
31
32 begin
33     process(clk)
34     begin
35         if rising_edge(clk) then
36             if en = '1' and MemWrite = '1' then
37                 RAM(conv_integer(ALUResin(7 downto 2))) <= RD2;
38             end if;
39         end if;
40     end process;
41     MemData <= RAM(conv_integer(ALUResin(7 downto 2)));
42     ALUResout <= ALUResin;
43 end Behavioral;

```

5.6 UC.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity UC is
5      Port ( Instr_opcode : in  STD_LOGIC_VECTOR (5 downto 0);
6            RegDst       : out STD_LOGIC;
7            ExtOp        : out STD_LOGIC;
8            ALUSrc       : out STD_LOGIC;
9            Branch       : out STD_LOGIC;
10           BranchNotEq  : out STD_LOGIC;
11           Jump         : out STD_LOGIC;
12           ALUOp        : out STD_LOGIC_VECTOR (1 downto 0);
13           MemWrite     : out STD_LOGIC;
14           MemtoReg     : out STD_LOGIC;
15           RegWrite     : out STD_LOGIC);
16 end UC;
17
18 architecture Behavioral of UC is
19 begin
20     process(Instr_opcode)
21     begin
22         RegDst <= '0'; ExtOp <= '0'; ALUSrc <= '0'; Branch <= '0';
23         BranchNotEq <= '0'; Jump <= '0'; MemWrite <= '0'; MemtoReg <= '0';
24         RegWrite <= '0'; ALUOp <= "00";
25
26         case Instr_opcode is
27             when "000000" => RegDst <= '1'; RegWrite <= '1'; ALUOp <= "10";
28             when "001000" => ExtOp <= '1'; ALUSrc <= '1'; RegWrite <= '1';
29                 ALUOp <= "00";
30             when "100011" => ExtOp <= '1'; ALUSrc <= '1'; MemtoReg <= '1';
31                 RegWrite <= '1'; ALUOp <= "00";
32             when "101011" => ExtOp <= '1'; ALUSrc <= '1'; MemWrite <= '1';
33                 ALUOp <= "00";
34             when "000100" => ExtOp <= '1'; Branch <= '1'; ALUOp <= "01";
35             when "000101" => ExtOp <= '1'; BranchNotEq <= '1'; ALUOp <= "01";
36             ;
37             when "000010" => Jump <= '1';

```

```

34         when others => null;
35     end case;
36 end process;
37 end Behavioral;

```

5.7 test_env.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity test_env is
6      Port ( clk : in  STD_LOGIC;
7            btn : in  STD_LOGIC_VECTOR (4 downto 0);
8            sw  : in  STD_LOGIC_VECTOR (15 downto 0);
9            led  : out STD_LOGIC_VECTOR (15 downto 0);
10           an   : out STD_LOGIC_VECTOR (7  downto 0);
11           cat  : out STD_LOGIC_VECTOR (6  downto 0));
12 end test_env;
13
14 architecture Behavioral of test_env is
15     component IFetch is
16         Port ( clk, rst, en : in  STD_LOGIC;
17               BranchAddress, JumpAddress : in  STD_LOGIC_VECTOR (31 downto
18                   0);
19               Jump, PCSrc : in  STD_LOGIC;
20               Instruction, PC_plus_4 : out STD_LOGIC_VECTOR (31 downto 0));
21     end component;
22
23     component UC is
24         Port ( Instr_opcode : in  STD_LOGIC_VECTOR (5 downto 0);
25               RegDst, ExtOp, ALUSrc, Branch, BranchNotEq, Jump : out
26                   STD_LOGIC;
27               ALUOp : out STD_LOGIC_VECTOR (1 downto 0);
28               MemWrite, MemtoReg, RegWrite : out STD_LOGIC);
29     end component;
30
31     component IDecode is
32         Port ( clk, en : in  STD_LOGIC;
33               Instr : in  STD_LOGIC_VECTOR (25 downto 0);
34               WD : in  STD_LOGIC_VECTOR (31 downto 0);
35               RegWrite, RegDst, ExtOp : in  STD_LOGIC;
36               RD1, RD2, Ext_Imm : out STD_LOGIC_VECTOR (31 downto 0);
37               func : out STD_LOGIC_VECTOR (5 downto 0);
38               sa : out STD_LOGIC_VECTOR (4 downto 0));
39     end component;
40
41     component EX is
42         Port ( PC_plus_4, RD1, RD2, Ext_Imm : in  STD_LOGIC_VECTOR (31 downto
43             0);
44               ALUSrc : in  STD_LOGIC;
45               ALUOp : in  STD_LOGIC_VECTOR (1 downto 0);
46               func : in  STD_LOGIC_VECTOR (5 downto 0);
47               sa : in  STD_LOGIC_VECTOR (4 downto 0);
48               BranchAddress, ALURes : out STD_LOGIC_VECTOR (31 downto 0);
49               Zero : out STD_LOGIC);
50     end component;
51
52     component MEM is

```

```

50     Port ( clk, en, MemWrite : in STD_LOGIC;
51           ALUResin, RD2 : in STD_LOGIC_VECTOR (31 downto 0);
52           MemData, ALUResout : out STD_LOGIC_VECTOR (31 downto 0));
53 end component;
54
55 component MPG is
56     Port ( enable : out STD_LOGIC;
57           btn, clk : in STD_LOGIC);
58 end component;
59
60 component SSD is
61     Port ( clk : in STD_LOGIC;
62           digits : in STD_LOGIC_VECTOR(31 downto 0);
63           an : out STD_LOGIC_VECTOR(7 downto 0);
64           cat : out STD_LOGIC_VECTOR(6 downto 0));
65 end component;
66
67 signal en, rst : STD_LOGIC;
68 signal Instruction, PC_plus_4 : STD_LOGIC_VECTOR(31 downto 0);
69 signal RegDst, ExtOp, ALUSrc, Branch, BranchNotEq, Jump, MemWrite,
70       MemtoReg, RegWrite : STD_LOGIC;
71 signal ALUOp : STD_LOGIC_VECTOR(1 downto 0);
72 signal RD1, RD2, Ext_Imm : STD_LOGIC_VECTOR(31 downto 0);
73 signal func : STD_LOGIC_VECTOR(5 downto 0);
74 signal sa : STD_LOGIC_VECTOR(4 downto 0);
75 signal BranchAddress, ALURes, MemData, ALUResout, WD, JumpAddress :
76       STD_LOGIC_VECTOR(31 downto 0);
77 signal Zero, PCSrc : STD_LOGIC;
78 signal digits_out : STD_LOGIC_VECTOR(31 downto 0);
79
80 begin
81     empege: MPG port map (enable => en, btn => btn(0), clk => clk);
82     rst <= btn(1);
83     display: SSD port map (clk => clk, digits => digits_out, an => an, cat
84         => cat);
85
86     inst_IFetch: IFetch port map (clk, rst, en, BranchAddress, JumpAddress,
87         Jump, PCSrc, Instruction, PC_plus_4);
88     inst_UC: UC port map (Instruction(31 downto 26), RegDst, ExtOp, ALUSrc,
89         Branch, BranchNotEq, Jump, ALUOp, MemWrite, MemtoReg, RegWrite);
90     inst_IDeode: IDeode port map (clk, en, Instruction(25 downto 0), WD,
91         RegWrite, RegDst, ExtOp, RD1, RD2, Ext_Imm, func, sa);
92     inst_EX: EX port map (PC_plus_4, RD1, RD2, Ext_Imm, ALUSrc, ALUOp, func,
93         sa, BranchAddress, ALURes, Zero);
94     inst_MEM: MEM port map (clk, en, MemWrite, ALURes, RD2, MemData,
95         ALUResout);
96
97     WD <= MemData when MemtoReg = '1' else ALUResout;
98     PCSrc <= (Branch and Zero) or (BranchNotEq and not Zero);
99     JumpAddress <= PC_plus_4(31 downto 28) & Instruction(25 downto 0) & "00"
100         ;
101
102     led(0) <= RegDst; led(1) <= ExtOp; led(2) <= ALUSrc; led(3) <= Branch;
103     led(4) <= BranchNotEq; led(5) <= Jump; led(6) <= MemWrite; led(7) <=
104         MemtoReg;
105     led(8) <= RegWrite; led(10 downto 9) <= ALUOp; led(15 downto 11) <= (
106         others => '0');
107
108     process(sw(7 downto 5), Instruction, PC_plus_4, RD1, RD2, Ext_Imm,
109         ALURes, MemData, WD)

```



```

98     begin
99         case sw(7 downto 5) is
100             when "000" => digits_out <= Instruction;
101             when "001" => digits_out <= PC_plus_4;
102             when "010" => digits_out <= RD1;
103             when "011" => digits_out <= RD2;
104             when "100" => digits_out <= Ext_Imm;
105             when "101" => digits_out <= ALURes;
106             when "110" => digits_out <= MemData;
107             when "111" => digits_out <= WD;
108             when others => digits_out <= (others => '0');
109         end case;
110     end process;
111 end Behavioral;

```

6 Single-Cycle Execution Trace

In the first iteration, index $i = 0$, and the value read from memory is $x[0] = 0$.

Step	SW(7:5)	"000"	"001"	"010"	"011"	"100"	"101"	"110"	"111"	Only for branch	
	Instr (assembly)	Instr (hex)	PC+4	RD1	RD2	Ext_Imm	ALURes	MemData	WD	BranchAddr	JumpAddr
0	addi \$1, \$0, 2	20010002	00000004	00000000	00000000	00000002	00000002	XXXXXXXX	00000002	XXXXXXXX	XXXXXXXX
1	addi \$2, \$0, 90	2002005A	00000008	00000000	00000000	0000005A	0000005A	XXXXXXXX	0000005A	XXXXXXXX	XXXXXXXX
2	addi \$3, \$0, 7	20030007	0000000C	00000000	00000000	00000007	00000007	XXXXXXXX	00000007	XXXXXXXX	XXXXXXXX
3	add \$4, \$0, \$0	00002020	00000010	00000000	00000000	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	XXXXXXXX
4	add \$5, \$0, \$0	00002820	00000014	00000000	00000000	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	XXXXXXXX
5	add \$6, \$0, \$0	00003020	00000018	00000000	00000000	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	XXXXXXXX
6	slt \$7, \$6, \$3	00C3382A	0000001C	00000000	00000007	XXXXXXXX	00000001	XXXXXXXX	00000001	XXXXXXXX	XXXXXXXX
7	beq \$7, \$0, end	10E0000F	00000020	00000001	00000000	0000000F	00000001	XXXXXXXX	XXXXXXXX	0000005C	XXXXXXXX
8	sll \$9, \$6, 2	00064880	00000024	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	XXXXXXXX
9	add \$9, \$4, \$9	00894820	00000028	00000000	00000000	XXXXXXXX	00000000	XXXXXXXX	00000000	XXXXXXXX	XXXXXXXX
10	lw \$8, 0(\$9)	8D280000	0000002C	00000000	00000000	00000000	00000000	00000000	00000000	XXXXXXXX	XXXXXXXX
11	addi \$6, \$6, 1	20C60001	00000030	00000000	XXXXXXXX	00000001	00000001	XXXXXXXX	00000001	XXXXXXXX	XXXXXXXX
12	slt \$7, \$8, \$1	0101382A	00000034	00000000	00000002	XXXXXXXX	00000001	XXXXXXXX	00000001	XXXXXXXX	XXXXXXXX
13	bne \$7, \$0, loop	14E0FFF8	00000038	00000001	00000000	FFFFFFF8	00000001	XXXXXXXX	XXXXXXXX	00000018	XXXXXXXX
— Second iteration (resume loop_start) —											
14	slt \$7, \$6, \$3	00C3382A	0000003C	00000001	00000007	XXXXXXXX	00000001	XXXXXXXX	00000001	XXXXXXXX	XXXXXXXX

Table 3: Execution trace (First full iteration)


Part II

Pipelined Implementation

This part details the transformation of the processor into a 5-stage pipeline architecture (IF, ID, EX, MEM, WB) to improve instruction throughput by allowing multiple instructions to be processed simultaneously.

7 Pipeline Registers and Architecture

 To support simultaneous instruction execution, intermediate registers were introduced between the processing stages to propagate data and control signals synchronously. The structural decision to resolve the destination register in the EX stage was implemented, moving the `RegDst` multiplexer appropriately.



[Placeholder: MIPS Pipeline Datapath Diagram]

Figure 9: MIPS Pipeline Architecture Datapath

REG_IF_ID [63:0]	REG_ID_EX [157:0]	REG_EX_MEM [106:0]	REG_MEM_WB [70:0]
Instruction [63:32]	MemToReg [157]	MemToReg [106]	MemToReg [70]
PC_plus_4 [31:0]	RegWrite [156]	RegWrite [105]	RegWrite [69]
	MemWrite [155]	MemWrite [104]	MemData [68:37]
	Branch [154]	Branch [103]	ALUResout [36:5]
	BranchNotEq [153]	BranchNotEq [102]	WA [4:0]
	ALUOp [152:151]	BranchAddress [101:70]	
	ALUSrc [150]	Zero [69]	
	RegDst [149]	ALURes [68:37]	
	PC_plus_4 [148:117]	RD2 [36:5]	
	RD1 [116:85]	WA [4:0]	
	RD2 [84:53]		
	Ext_Imm [52:21]		
	func [20:15]		
	sa [14:10]		
	rt [9:5]		
	rd [4:0]		

Table 4: Bit-level mapping of the Pipeline Registers

8 Pipeline Control Signals

The control signals generated by the Control Unit are propagated synchronously through the pipeline registers. The table below details the signals for the supported instructions, including the specific **BranchNotEq** signal used for the **bne** instruction.

Instruction	Opcode [31-26]	RegDst	ExtOp	ALUSrc	Branch	Br_ne	Jump	MemWrite	MemtoReg	RegWrite	ALUOp[1:0]	function [5-0]	ALUCtrl[2:0]
add	000000	1	0	0	0	0	0	0	0	1	10	100000	000 (+)
and	000000	1	0	0	0	0	0	0	0	1	10	100100	010 (&)
slt	000000	1	0	0	0	0	0	0	0	1	10	101010	011 (<)
sll	000000	1	0	0	0	0	0	0	0	1	10	000000	100 (<<)
addi	001000	0	1	1	0	0	0	0	0	1	00 (+)	X	000 (+)
lw	100011	0	1	1	0	0	0	0	1	1	00 (+)	X	000 (+)
sw	101011	0	1	1	0	0	0	1	0	0	00 (+)	X	000 (+)
beq	000100	X	1	0	1	0	0	0	X	0	01 (-)	X	001 (-)
bne	000101	X	1	0	0	1	0	0	X	0	01 (-)	X	001 (-)
j	000010	X	X	X	0	0	1	0	X	0	XX	X	000

Table 5: Instruction encodings and control signals mapping

9 Hazard Resolution

The overlapping of instructions introduced Data Hazards (Read-After-Write) and Control Hazards (Branch/Jump). Since the architecture does not implement a hardware Forwarding Unit, hazards were resolved through software by inserting **NoOp** (No Operation) instructions into the machine code.

- **Data Hazards (RAW):** Writing to the register file occurs in the **WB** stage. Reading occurs in the **ID** stage. Up to 2 **NoOp** instructions are required to align the **ID** stage of a dependent instruction with the **WB** stage of the producer.
- **Control Hazards (Branch):** The decision for **beq** and **bne** is evaluated in the **MEM** stage. Therefore, 3 **NoOp** instructions (Delay Slots) are inserted after each conditional branch to prevent fetching incorrect instructions.
- **Control Hazards (Jump):** The target address is computed in the **ID** stage, requiring only 1 **NoOp** instruction.

10 Pipeline Execution Trace

10.1 Ideal Execution (Hazard Identification)

The table below illustrates the theoretical execution of the first loop iteration assuming no stalls. Structural (S), Data (D), and Control (C) hazards are explicitly marked in the stages where they occur, specifying the dependent instruction addresses.

Poz.	Instrucțiune	C1	C2	C3	C4	C5	C6	C7	C8	C9	C10	C11	C12	C13	C14	C15	C16	C17	C18	C19	C20	C21	C22	C23	C24	C25	C26	C27
0	addi \$1, \$0, 2	IF	ID	EX	MEM	WB																						
1	addi \$2, \$0, 90		IF	ID	EX	MEM	WB																					
2	addi \$3, \$0, 7			IF	ID	EX	MEM	WB																				
3	add \$4, \$0, \$0				IF	ID	EX	MEM	WB																			
4	add \$5, \$0, \$0					IF	ID	EX	MEM	WB																		
5	add \$6, \$0, \$0						IF	ID	EX	MEM	WB(\$6-D:6)																	
6	slt \$7, \$6, \$3							IF	ID(\$6)	EX	MEM	WB(\$7-D:7)																
7	beq \$7, \$0, end								IF	ID(\$7)	EX	MEM(C)	WB															
8	add \$9, \$4, \$6									IF	ID	EX	MEM	WB(\$9-D:9)														
9	lw \$8, 0(\$9)										IF	ID(\$9)	EX	MEM	WB(\$8-D:11)													
10	addi \$6, \$6, 1											ID	EX	MEM	WB													
11	slt \$7, \$8, \$1												ID	EX	MEM	WB(\$7-D:12..14)												
12	bne \$7, \$0, loop												IF	ID(\$8)	EX	MEM(C)	WB											
13	slt \$7, \$2, \$8													ID	EX	MEM	WB(\$7-D:14..16)											
14	bne \$7, \$0, loop													IF	ID(\$7)	EX	MEM(C)	WB										
15	slt \$7, \$0, \$8														ID	EX	MEM	WB(\$7-D:16)										
16	beq \$7, \$0, loop														IF	ID(\$7)	EX	MEM(C)	WB									
17	addi \$9, \$8, -1																											
18	and \$9, \$8, \$9																											
19	bne \$9, \$0, loop																											
20	add \$5, \$5, \$8																											
21	j loop_start																											
22	j end																											

Table 6: Ideal execution highlighting structural, data, and control hazards

[illegible]

Table 7: Resolved pipeline execution showing 61 clock cycles required for the first complete loop iteration

11 VHDL Code Modifications (Pipeline)

The datapath was adapted to carry signals through the intermediate pipeline registers. Port interfaces for IDecode and EX modules were updated to reflect the physical relocation of the Write Address calculation logic.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity test_env_pipeline is
6      Port ( clk : in  STD_LOGIC;
7            btn : in  STD_LOGIC_VECTOR (4 downto 0);
8            sw  : in  STD_LOGIC_VECTOR (15 downto 0);
9            led : out STD_LOGIC_VECTOR (15 downto 0);
10           an  : out STD_LOGIC_VECTOR (7  downto 0);
11           cat : out STD_LOGIC_VECTOR (6  downto 0));
12 end test_env_pipeline;
13
14 architecture Behavioral of test_env_pipeline is
15     -- Component declarations (IFetch, UC, IDecode, EX, MEM, MPG, SSD)
16     -- omitted for brevity
17
18     -- Inter-stage signals
19     signal en, rst : STD_LOGIC;
20     signal Instruction, PC_plus_4 : STD_LOGIC_VECTOR(31 downto 0);
21     signal PCSrc, Jump : STD_LOGIC;
22     signal JumpAddress : STD_LOGIC_VECTOR(31 downto 0);
23     signal RegDst, ExtOp, ALUSrc, Branch, BranchNotEq, MemWrite, MemtoReg,
24         RegWrite : STD_LOGIC;
25     signal ALUOp : STD_LOGIC_VECTOR(1 downto 0);
26     signal RD1, RD2, Ext_Imm : STD_LOGIC_VECTOR(31 downto 0);
27     signal func : STD_LOGIC_VECTOR(5 downto 0);
28     signal sa : STD_LOGIC_VECTOR(4 downto 0);
29     signal BranchAddress, ALURes, MemData, ALUResout : STD_LOGIC_VECTOR(31
30         downto 0);
31     signal Zero : STD_LOGIC;
32     signal WA_out_EX : STD_LOGIC_VECTOR(4 downto 0);
33     signal WD : STD_LOGIC_VECTOR(31 downto 0);
34
35     -- PIPELINE REGISTERS
36     -- 1. IF/ID
37     signal IF_ID_PC_plus_4, IF_ID_Instr : STD_LOGIC_VECTOR(31 downto 0);
38
39     -- 2. ID/EX
40     signal ID_EX_PC_plus_4, ID_EX_RD1, ID_EX_RD2, ID_EX_Ext_Imm :
41         STD_LOGIC_VECTOR(31 downto 0);
42     signal ID_EX_func : STD_LOGIC_VECTOR(5 downto 0);
43     signal ID_EX_sa, ID_EX_rt, ID_EX_rd : STD_LOGIC_VECTOR(4 downto 0);
44     signal ID_EX_RegDst, ID_EX_ALUSrc, ID_EX_Branch, ID_EX_BranchNotEq,
45         ID_EX_MemWrite, ID_EX_MemtoReg, ID_EX_RegWrite : STD_LOGIC;
46     signal ID_EX_ALUOp : STD_LOGIC_VECTOR(1 downto 0);
47
48     -- 3. EX/MEM
49     signal EX_MEM_BranchAddress, EX_MEM_ALURes, EX_MEM_RD2 :
50         STD_LOGIC_VECTOR(31 downto 0);
51     signal EX_MEM_Zero, EX_MEM_Branch, EX_MEM_BranchNotEq, EX_MEM_MemWrite,
52         EX_MEM_MemtoReg, EX_MEM_RegWrite : STD_LOGIC;
53     signal EX_MEM_WA : STD_LOGIC_VECTOR(4 downto 0);
```



```

48  -- 4. MEM/WB
49  signal MEM_WB_MemData, MEM_WB_ALURes : STD_LOGIC_VECTOR(31 downto 0);
50  signal MEM_WB_WA : STD_LOGIC_VECTOR(4 downto 0);
51  signal MEM_WB_MemtoReg, MEM_WB_RegWrite : STD_LOGIC;
52
53  begin
54      -- MPG, SSD and Module instantiations mapped to pipeline signals...
55
56      process(clk)
57      begin
58          if rising_edge(clk) then
59              if en = '1' then
60                  -- IF -> ID
61                  IF_ID_PC_plus_4 <= PC_plus_4;
62                  IF_ID_Instr      <= Instruction;
63
64                  -- ID -> EX
65                  ID_EX_PC_plus_4 <= IF_ID_PC_plus_4;
66                  ID_EX_RD1       <= RD1;
67                  ID_EX_RD2       <= RD2;
68                  ID_EX_Ext_Imm    <= Ext_Imm;
69                  ID_EX_func      <= func;
70                  ID_EX_sa        <= sa;
71                  ID_EX_rt        <= IF_ID_Instr(20 downto 16);
72                  ID_EX_rd        <= IF_ID_Instr(15 downto 11);
73
74                  ID_EX_RegDst     <= RegDst;
75                  ID_EX_ALUSrc    <= ALUSrc;
76                  ID_EX_ALUOp     <= ALUOp;
77                  ID_EX_Branch    <= Branch;
78                  ID_EX_BranchNotEq <= BranchNotEq;
79                  ID_EX_MemWrite  <= MemWrite;
80                  ID_EX_MemtoReg  <= MemtoReg;
81                  ID_EX_RegWrite  <= RegWrite;
82
83                  -- EX -> MEM
84                  EX_MEM_BranchAddress <= BranchAddress;
85                  EX_MEM_ALURes       <= ALURes;
86                  EX_MEM_RD2          <= ID_EX_RD2;
87                  EX_MEM_Zero        <= Zero;
88                  EX_MEM_WA          <= WA_out_EX;
89
90                  EX_MEM_Branch       <= ID_EX_Branch;
91                  EX_MEM_BranchNotEq  <= ID_EX_BranchNotEq;
92                  EX_MEM_MemWrite     <= ID_EX_MemWrite;
93                  EX_MEM_MemtoReg     <= ID_EX_MemtoReg;
94                  EX_MEM_RegWrite     <= ID_EX_RegWrite;
95
96                  -- MEM -> WB
97                  MEM_WB_MemData      <= MemData;
98                  MEM_WB_ALURes       <= ALUResout;
99                  MEM_WB_WA           <= EX_MEM_WA;
100
101                  MEM_WB_MemtoReg     <= EX_MEM_MemtoReg;
102                  MEM_WB_RegWrite     <= EX_MEM_RegWrite;
103              end if;
104          end if;
105      end process;
106
107      WD <= MEM_WB_MemData when MEM_WB_MemtoReg = '1' else MEM_WB_ALURes;

```

```
108     PCSrc <= (EX_MEM_Branch and EX_MEM_Zero) or (EX_MEM_BranchNotEq and not
        EX_MEM_Zero);
109     JumpAddress <= IF_ID_PC_plus_4(31 downto 28) & IF_ID_Instr(25 downto 0)
        & "00";
110
111 end Behavioral;
```

test_env_pipeline.vhd (Top-Level Pipeline)

Part III

Conclusions

12 FPGA Synthesis

Both architectures (Single-Cycle and Pipelined) were synthesized successfully in the Vivado environment. The resulting `.bit` files were programmed onto the FPGA board. The execution proved logically sound, correctly validating the conditional algorithms, executing conditional branches (`beq`, `bne`), arithmetic logic, and accurately accumulating the sum of valid elements while resolving inherent control and data pipeline hazards through the proper insertion of machine code NOPs.